

Lab 02: Verilog Simulator (VCS) (1%)

Assigned on Sep 11, 2025

Due day on **Sep 18, 2025**

Objective

In this lab, you will learn:

1. Verilog HDL coding for basic digital circuit elements.
2. Construct a simple ALU with synthesizable Verilog HDL.
3. Simulate Verilog circuit with simulator VCS.

Demo checklist:

- ☐ Schematic view of your ALU.
- ☐ Simulation result of ALU.
- ☐ Spyglass clean.
- ☐ Answer the following question.
 1. Why do we need combinational part and sequential part for digital circuits?
 2. What's the difference between combinational and sequential circuits in implementation?

Environment Setup

Copy lab file packages from ee4292. Decompress the package and enter it. You can check the file list in Appendix.

```
$ cp ~ee4292/iclab2025/lab02.zip .
```

```
$ unzip lab02.zip
```

```
$ cd lab02
```

Description

Open the files in reference with *Verdi*. You will find some Verilog example for the basic digital elements. Besides, you can also find suggestions for using these elements in comment. Follow the coding styles in the reference and what you learn in class, and then construct an ALU.

Figure 1 is a simple ALU with two 8-bit input signals and six instructions. You can input signals and select the functions with instruction. The functions and their corresponding instructions are defined in Table 1.

 


Figure 1. ALU architecture.

Instruction[3:0]	Function
4'b0000	Addition
4'b0001	Subtraction($A-B$)
4'b0010	B Inversion
4'b0011	AND
4'b0100	OR
default	Exclusive OR

Table 1. ALU function table.

Action Items

I. View the schematic of basic elements.

1. Open Verdi to view the schematic diagram.
\$ verdi &
2. Open *basic_elements.v* in reference with Verdi.

II. Construct the ALU.

1. Open *lab2_alu.v* with the text editor (i.e. *gedit*, *vim* etc.).
2. Construct the ALU described in Figure 1. Start from the module template *lab2_alu.v*, which defines the I/O of the module.
3. Run VCS Simulator to do lint for Verilog and fix all of the language errors and warnings with the messages shown on the terminal.

```
$ vcs -full64 lab2_alu.v
```

III. Run simulation with testbench.

Run simulation with the following command.

```
$ vcs lab2_alu_test.v lab2_alu.v -R -full64 -debug_access+all +v2k
```

or

```
$ vcs -f lab2_run.f -R -full64 -debug_access+all +v2k
```

IV. Run synthesizable check with *spyglass*.

1. Run *spyglass* in terminal. Click *Add Files* import files, select *lint* and *adv_lint* in *Goal Setup*. Press *Run Goals* button and you may check the code is synthesizable or not.

```
$ spyglass &
```

2. Fix all the errors and warnings.

Appendix

Filename	Description
lab2_alu.v	RTL code for ALU
lab2_alu_test.v	Test bench for ALU
lab2_run.f	Filelist
golden.dat	Correct respond
reference/	Verilog example code